

5.3-5


(2)

$$A_{V1} = \frac{V_2}{V_{IN}} = \frac{R}{R} + 1 = 2$$

$$A_{V2} = \frac{V_{OUT}}{V_2} = \frac{R}{3R + R} = \frac{1}{4}$$

$$A_V = \frac{V_{OUT}}{V_{IN}} = A_{V1} A_{V2} = \frac{1}{2}$$

$$G_V = -6\text{dB}$$

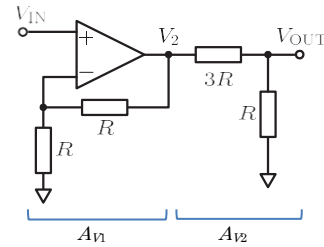


(3)

$$A_{V1} = \frac{V_1}{V_{IN}} = \frac{R}{R + R} = \frac{1}{2}$$

$$A_{V2} = \frac{V_{OUT}}{V_1} = \frac{R}{R} + 1 = 2$$

$$A_V = \frac{V_{OUT}}{V_{IN}} = A_{V1} A_{V2} = 1$$


$$G_V = 0\text{dB}$$

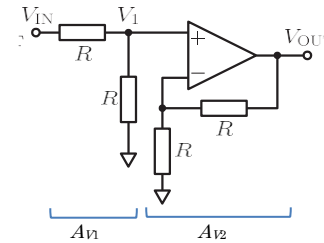

(3)


$$A_V = \frac{V_{OUT}}{V_{IN}} = \frac{R}{R} + 1 = 2$$

$$G_V = 6\text{dB}$$

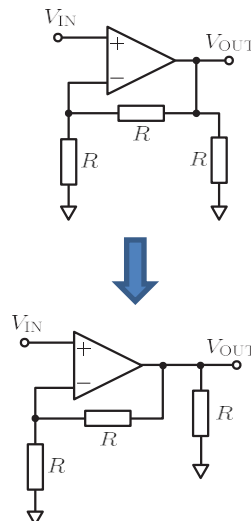


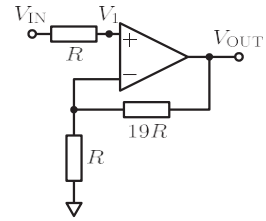
(5)

$$V_{IN} = V_1$$
$$A_v = \frac{V_{OUT}}{V_{IN}} = \frac{19R}{R} + 1 = 20 = 2 \times 10$$
$$G_v = 2 + 20 = 26\text{dB}$$



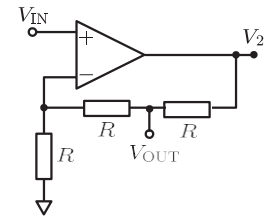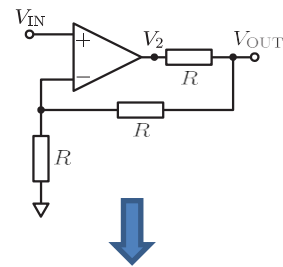(6)

$$A_{v1} = \frac{V_2}{V_{IN}} = \frac{2R}{R} + 1 = 3$$
$$A_v = \frac{V_{OUT}}{V_{IN}} = \frac{2}{3} \frac{V_2}{V_{IN}} = \frac{2}{3} A_{v1} = 2$$
$$G_v = 6\text{dB}$$




(7)

$$V_{IN} = V_1$$


R に電流が流れないので
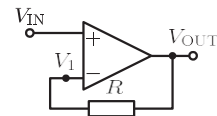
$$V_1 = V_{OUT}$$
$$A_v = \frac{V_{OUT}}{V_{IN}} = 1$$
$$G_v = 0\text{dB}$$



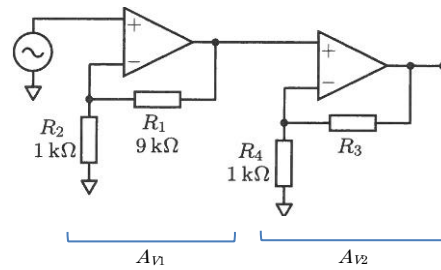
5.3-6

$G_V = 26\text{dB} \rightarrow A_V = 200$
 $A_{V1} = 10,$
 $A_V = A_{V1} A_{V2}$
 $A_{V2} = A_V / A_{V1} = 20$
 $A_{V2} = R_3 / R_4 + 1$
 $R_3 = R_4 (A_{V2} - 1) = 19\text{k}\Omega$




5.4-3

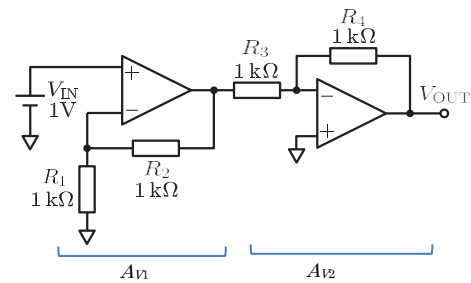(1)
 $A_{V1} = R_2 / R_1 + 1 = 2$
 $A_{V2} = -R_4 / R_3 = -1$
 $A_V = A_{V1} A_{V2} = -2$
 $V_{OUT} = A_V V_{IN} = -2\text{V}$
 $G_V = 6\text{dB}$




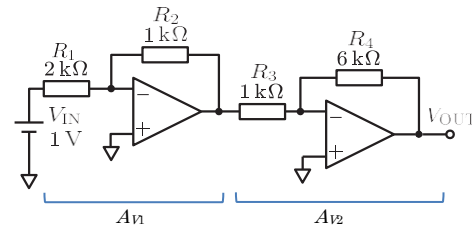(2)
 $A_{V1} = -R_2 / R_1 = -1/2$
 $A_{V2} = -R_4 / R_3 = -6$
 $A_V = A_{V1} A_{V2} = 3$
 $V_{OUT} = A_V V_{IN} = 3\text{V}$
 $G_V = 10\text{dB}$



(3)
 非反転入力端子に加わる電圧は、0V であり、
 図 5.29 と同様の回路として考える。

$A_V = -R_2 / R_1 = -100$
 $V_{OUT} = A_V V_{IN} = -100\text{V}$
 $|A_V| = 100 = 10 \times 10$
 $G_V = 20 + 20 = 40\text{dB}$

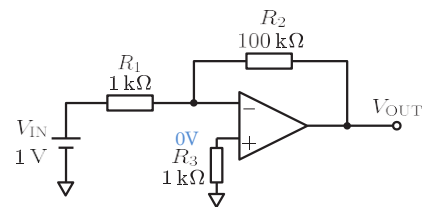

(4)

バーチャルショートにより,

反転入力端子の電圧は0Vである.

従って, R_3 に流れる電流は0Aであり,


R_3 は, 取り外して考えることができる.

$$A_v = -R_2 / R_1 = -10$$

$$V_{OUT} = A_v V_{IN} = -10V$$

$$|A_v| = 10$$

$$G_v = 20dB$$

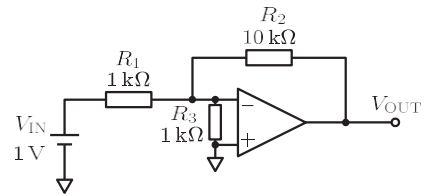

(5)

テブナンの定理を用いて回路を変形

$$A_v' = -R_4 / (R_3 + R_2) = -1$$


$$R' = R_1 / R_2 = 1k\Omega$$

$$V_{IN}' = V_{IN} / 2 = 1V$$


$$V_{OUT} = A_v' V_{IN}' = -1V$$

$$A_v = V_{OUT} / V_{IN} = -1/2$$

$$G_v = -6dB$$

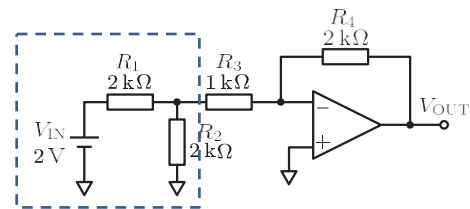

↓ テブナン

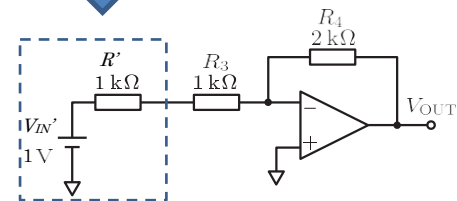

5.5-3

$$5.5-1 \text{ より } V_{OUT} = -(R_3 V_1 / R_1 + R_3 V_2 / R_2)$$

$$R_3 / R_2 = 3 \text{ より, } R_3 = 3R_2 = 3k\Omega$$

$$R_3 / R_1 = 2 \text{ より, } R_1 = R_2 / 2 = 1.5k\Omega$$

5.5-6

重ね合わせの理を用いて解く

< V_1 のみで考える >

イマジナリーショートより $V_a=0V$ のため, R_2 は無視できる.

$$V_{OUT}' = -R_5 V_1 / R_1 = -V_1$$

< V_2 のみで考える >

$$V_{OUT}'' = -R_5 V_2 / R_2 = -V_2$$

< V_3 のみで考える >

$$V_b = \frac{(R_4 // R_6)}{R_3 + (R_4 // R_6)} V_3 = \frac{1}{3} V_3$$



$$V_{OUT}''' = \left(\frac{R_5}{R_1 // R_2} + 1 \right) V_b = 3V_b = V_3$$

< V_4 のみで考える >

V_3 と同様に考えると

$$V_{OUT}'''' = V_4$$
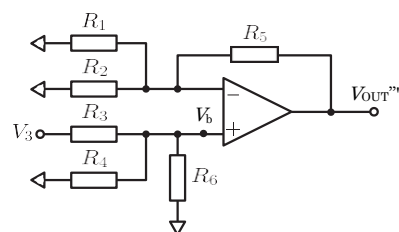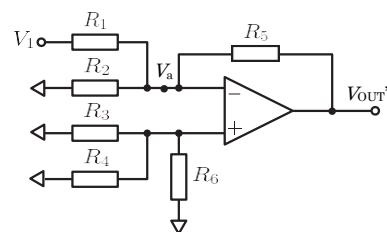
$$V_{OUT} = V_{OUT}' + V_{OUT}'' + V_{OUT}''' + V_{OUT}'''' = -V_1 - V_2 + V_3 + V_4$$



5.5-7

重ね合わせの理で考える

< V_0 のみで考える >

$$V_0 = 1V \text{ のとき } V_{OUT}' = -R_4 V_0 / R_1 = -1V$$

$$V_0 = 0V \text{ のとき } V_{OUT}' = 0V$$

< V_1 のみで考える >

$$V_1 = 1V \text{ のとき } V_{OUT}'' = -R_4 V_1 / R_2 = -2V$$

$$V_1 = 0V \text{ のとき } V_{OUT}'' = 0V$$

< V_2 のみで考える >

$$V_2 = 1V \text{ のとき } V_{OUT}''' = -R_4 V_2 / R_3 = -4V$$

$$V_2 = 0V \text{ のとき } V_{OUT}''' = 0V$$

$$V_{OUT} = V_{OUT}' + V_{OUT}'' + V_{OUT}'''$$