

8.1-2

(a)


$$I_B = \frac{E - V_{BE}}{R_E' + R_B} = \frac{E - V_{BE}}{h_{FE} R_E + R_B}$$

$$V_1 = I_B R_E' = I_B h_{FE} R_E = \frac{h_{FE} R_E}{h_{FE} R_E + R_B} (E - V_{BE})$$

$$R_B \ll h_{FE} R_E \text{ より}$$

$$V_1 \approx E - V_{BE} = 4.3V$$

$$V_B = V_1 + V_{BE} = 5V$$

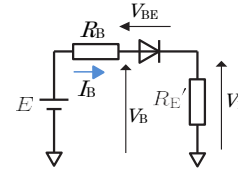


(b)

$$I_B = \frac{E - V_{BE}}{R_E' + R_B} = \frac{E - V_{BE}}{h_{FE} R_E + R_B}$$

$$V_2 = I_B h_{FE} R_E = \frac{h_{FE} R_E}{h_{FE} R_E + R_B} (E - V_{BE})$$

$$V_2 = 2.15V$$

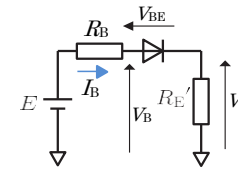


(c)

$R_B \ll h_{FE} R_E$ より (a) と同様に考えることができる.

$$V_B \doteq E = 5V$$

$$V_3 = 4.3V$$

テブナンの定理より

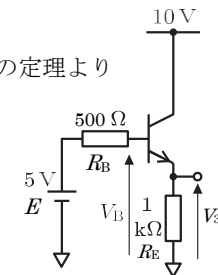

(d)


$$(c) \text{ より } V_B = V_{CC}/2 \doteq 5V$$

$$V_3 = V_B - V_{BE}$$

$$I_E = V_3 / R_E$$

$$I_C \doteq I_E$$

$$V_4 = V_{CC} - R_C I_C = 5.7V$$

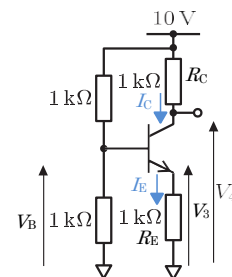

(2)

$$I_E = V_E / R_E$$

$$V_E = I_E R_E \doteq I_C R_E = 1V$$

$$V_B = V_E + V_{BE} = 1.7V$$

$R_2 \ll h_{FE} R_E$ のため、ベースの入力抵抗を無視する.

分圧の公式より

$$V_B \doteq R_2 V_{CC} / (R_1 + R_2)$$

$$R_1 = R_2 V_{CC} / V_B - R_2 = 9k\Omega$$

8.1-4

(1) $R_1=1k\Omega$

<交流のみで考える>

$$v_1 = \frac{h_{fe} R_E}{h_{fe} R_E + R_1 + h_{ie}} v_{in}$$


$h_{fe} R_E \gg R_1 + h_{ie}$ より

$$v_1 \approx v_{in} = 10mV$$

<直流のみで考える>

$$V_1' \doteq E - V_{BE} = 4V$$

$$V_1 = V_1' + v_1$$

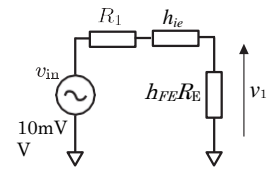

(2)

$R_1=99k\Omega$


<交流のみで考える>

$$v_1 = \frac{h_{fe} R_E}{h_{fe} R_E + R_1 + h_{ie}} v_{in} = 5mV$$

<直流のみで考える>

$$V_1' = (E - V_{BE}) h_{FE} R_E / (h_{FE} R_E + R_1) \doteq 2V$$

$$V_1 = V_1' + v_1$$

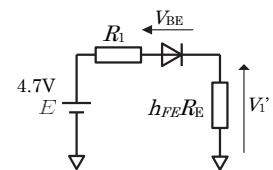


8.2-3

(1)

$$Z_{OUT1} = Z_0 + R_1 = h_{ie}/h_{fe} // R_E + R_1$$


$$h_{ie}/h_{fe} \ll R_E \text{ より}$$

$$Z_{OUT1} = h_{ie}/h_{fe} + R_1$$

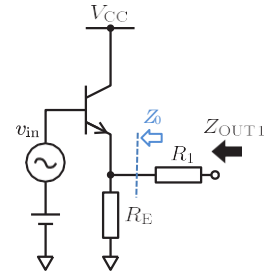

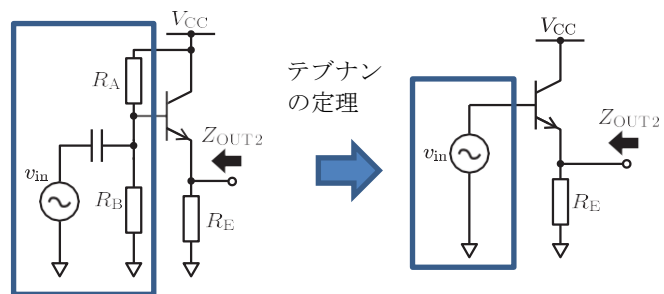
(2)

$$Z_{OUT2} = h_{ie}/h_{fe} // R_E \approx h_{ie}/h_{fe}$$



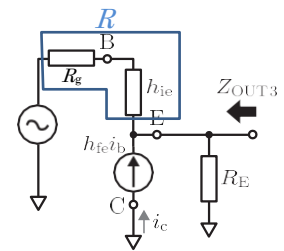(3)

$$Z_{OUT3} = R/h_{fe} // R_E = (h_{ie} + R_g)/h_{fe} // R_E$$



(4)

$$R_2 = R_g // R_A // R_B$$

$$Z_{OUT4}' = (R_2 + h_{ie})/h_{fe} // R_E$$

$$Z_{OUT4} = Z_{OUT4}' + R_1$$

