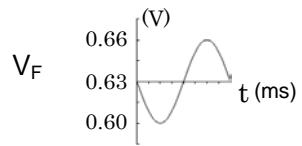


演習問題解答

1.2-2

$$V_1 = v + V_F \\ V_F = V_1 - v$$




1.3-4


右の図は、等価回路である。

$$(1) \quad V_2 = E - V_D = 10V$$
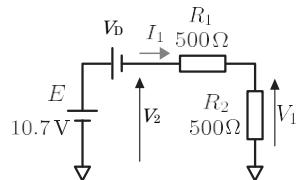
$$V_1 = \frac{R_2}{R_1 + R_2} V_2 = V_2 / 2 = 5V$$



$$(2) \quad I_1 = \frac{E}{R_2} = 10mA$$

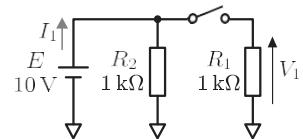


(3) 電流を流すには2つのダイオードに $2V_D$ 以上を加える必要がある。

$E > 2V_D$ より右図となる。


$$V_1 = E - V_D - V_D = 8.6V$$

$$I_1 = V_1 / R_1 = 8.6mA$$

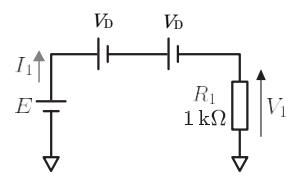


(4)

$E < 2V_D$ より右図となる。

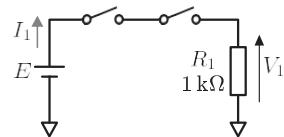


$$(5) \quad V_1 = E - V_D = 9.3V$$

$$I_1 = V_1 / R_1 = 9.3mA$$

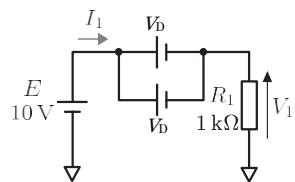


$$(6) \quad V_1 = E = 10V$$

$$I_1 = 0A$$

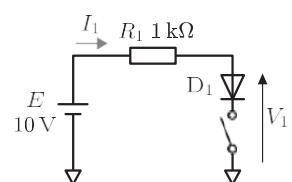
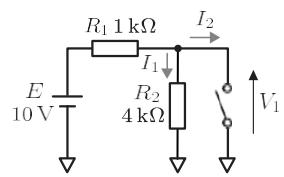
$$(7) \quad V_1 = \frac{R_2}{R_1 + R_2} E = 8V$$




$$(8) \quad V_1 = V_D = 0.7V$$

$$I_1 = V_1 / R_2 = 0.175mA$$

$$I_3 = \frac{E - V_1}{R_1} = 9.3mA$$


$$I_2 = I_3 - I_1 = 9.125mA$$

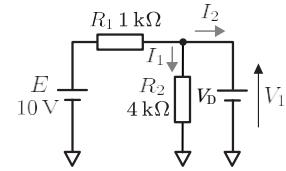

$$(9) \quad V_1 = \frac{R_2 E}{R_1 + R_2} = 0.5V$$

$$I_1 = V_1 / R_2 = 0.5mA$$

$$I_2 = 0A$$

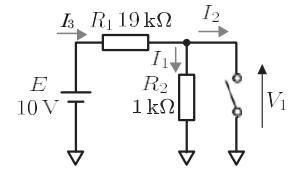


$$(10) \quad E = V_1 + V_D + V_{R1}$$

$$E = I_1 R_2 + V_D + I_1 R_1$$

$$I_1 = \frac{E - V_D}{R_1 + R_2} = 3.1mA$$


$$V_1 = I_1 R_2 = 6.2V$$

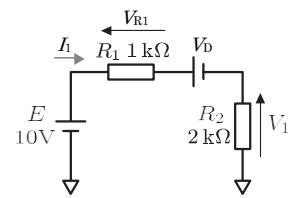

$$(11) \quad I_1 = \frac{E - V_D}{R_1 + R_2} = 3.1mA$$

$$V_{R2} = I_1 R_2 = 3.1V$$

$$V_1 = V_D + V_{R2} = 3.8V$$

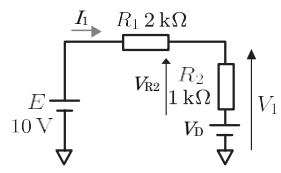


$$(12) \quad V_1 = E - V_D = 9.3V$$

$$I_2 = \frac{V_D}{R_1} = 0.7mA$$

$$I_3 = \frac{V_1}{R_2} = \frac{E - V_D}{R_2} = 9.3mA$$


$$I_1 = I_3 - I_2 = 8.6mA$$

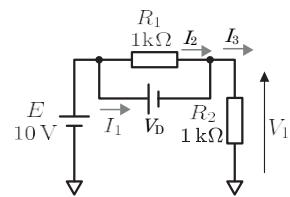


$$(13) \quad V_1 = V_D + V_2 = V_D + R_l I_0 = 2.7V$$

$$I_2 = \frac{V_D}{R_2} = 0.7mA$$

$$I_1 = I_0 - I_2 = 1.3mA$$

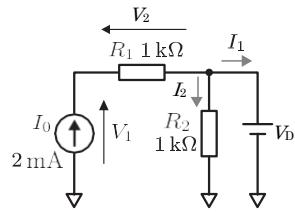
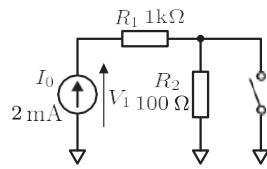
$$(14) \quad V_1 = I_0(R_1 + R_2) = 2.2V$$




(15) キルヒホップのノード解析を用いる

$$I_0 = I_1 + I_2$$

$$I_0 = \frac{V_1}{R_1} + \frac{V_1 - V_D}{R_2} \quad (1)$$


式(1)に値を入れて計算すると

$$V_1 = 1.7V$$

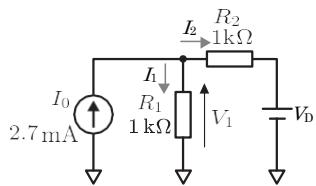


1.3-5

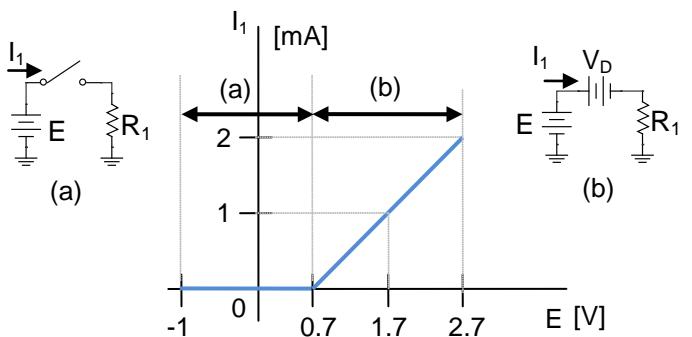- (1) ダイオードがスイッチ OFF と電圧源 V_D に置き換えた時をそれぞれ(a), (b)に示す。
 (a)において、電流 I_1 はゼロ
 (b)において、電流 I_1 は以下の式が成り立つ
 $I_1 = (E - V_D)/R_1$



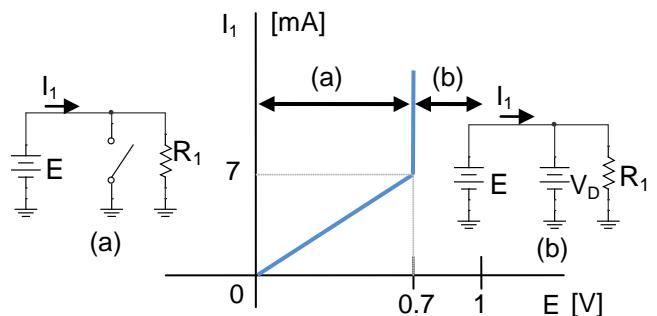
(2)

- (a)において、電流 I_1 は以下の式が成り立つ
 $I_1 = E/R_1$
 (b)において、電流 I_1 は ∞



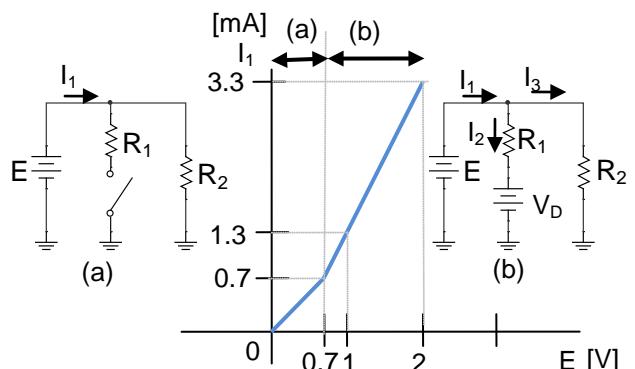
(3)

- (a)において、電流 I_1 は以下の式が成り立つ
 $I_1 = E/R_2$
 (b)において、各電流 $I_1 \sim I_3$ は以下の式が成り立つ
 $I_2 = (E - V_D)/R_1$
 $I_3 = E/R_2$
 $I_1 = I_2 + I_3$




1.5-4


(1) $V_1 = V_Z = 5V$

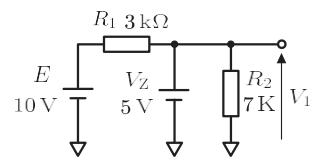


(2) $V_1 = R_2 E / (R_2 + R_1) = 3V$

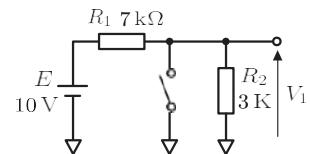


(3) $V_1 = V_{Z1} + V_{Z2} = 8V$

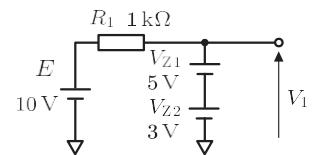

(4) $V_1 = V_{Z2} = 3V$

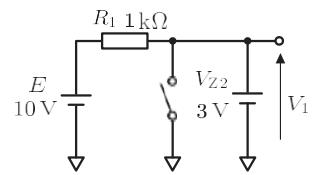

(5) $V_1 = V_D + V_{Z2} = 5.7V$

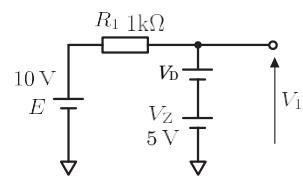

(6) $I_1 = (E - V_Z) / (R_1 + R_2) = 2.5mA$

$V_1 = V_Z + R_2 I_1 = 7.5V$

